

Electronic oscillator circuit

Philippe W. Courteille, 05/02/2021

Solution: a. The equation of motion of the damped and forced spring mass system is,

$$ma + bv + kx = F_0 \cos \omega t .$$

The solutions are,

$$\tan \delta = \frac{\sin \delta}{\cos \delta} = \frac{Im e^{i\delta}}{Re e^{i\delta}} = \frac{R\omega}{L(\omega_0^2 - \omega^2)}$$
$$A = |Ae^{-i\delta}| = \left| \frac{U_0 \omega}{L(\omega_0^2 - \omega^2) + i\omega R} \right| = \frac{U_0 \omega}{\sqrt{L^2(\omega_0^2 - \omega^2)^2 + R^2\omega^2}} .$$

b. The natural frequency is,

$$\omega_0 = \frac{1}{\sqrt{LC}} .$$

c. Quality factor can be increased by decreasing strength R ,

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} .$$